



EE141-Spring 2012 Digital Integrated Circuits

Lecture 18 Dynamic Logic

EECS141

Lecture #18

1


Administrativa

- ❑ Midterm 2 Graded!
- ❑ Project Phase 1 discussion
- ❑ Phase 2 Launch - Energy

EECS141

Lecture #18

2

 


Dynamic Logic

EECS141

Lecture #18

3


Dynamic Gate

 

Two phase operation

Precharge (Clk = 0)

Evaluate (Clk = 1)

 

EECS141

Lecture #18

4

tlh=zero, the result has been stored in CL. If we want to get one, we do not need to do anything. If we want to get zero, we discharge the CL.


Conditions on Output

- ❑ Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- ❑ Inputs to the gate can make **at most** one transition during evaluation.
- ❑ Output can be in the high impedance state during and after evaluation (PDN off), state is stored on C_L

Properties of Dynamic Gates

- ❑ Logic function is implemented by the PDN only
 - number of transistors is $N + 2$ (versus $2N$ for static complementary CMOS)
- ❑ Full swing outputs ($V_{OL} = \text{GND}$ and $V_{OH} = V_{DD}$)
- ❑ Non-ratioed - sizing of the devices does not affect the logic levels
- ❑ Faster switching speeds
 - reduced capacitance due to **lower input** capacitance (C_{in})
 - no I_{sc} , so all the current provided by PDN goes into discharging C_L
???

LE of Dynamic Gates

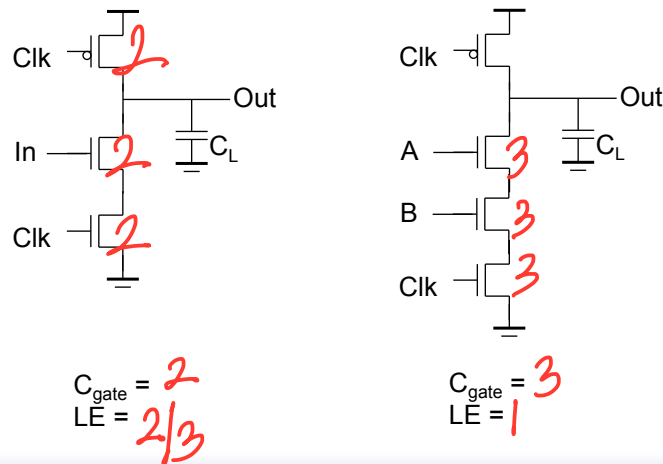

EECS141

Lecture #18

7

Previously, most chips used dynamic logics. But now, we only use a few of dynamic logic. The main reason is leakage.

Properties of Dynamic Gates

- ❑ Overall power dissipation usually **higher** than static CMOS
 - no static current path ever exists between V_{DD} and GND (including P_{sc})
 - no glitching
 - **higher transition probabilities**
 - **extra load on Clk**
- ❑ PDN starts to work as soon as the input signals exceed V_{Tn} , so V_M , V_{IH} and V_{IL} equal to V_{Tn}
 - low noise margin (NM_L)
- ❑ Needs a precharge/evaluate clock

EECS141

Lecture #18

8

$$\text{CMOS } C V_{DD}^2 \cdot P_{0 \rightarrow 1} f \quad P_{0 \rightarrow 1} = P_0 \cdot P_1$$

$$\text{Dynamic } C V_{DD}^2 P_0 \cdot f$$

Dynamic logic not allow glitch which will cause the voltage of CL down and happen in static logic.


Challenges of Dynamic Gates

□ Noise sensitivity and small noise margins


- Leakage
- Charge sharing
- Clock feedthrough

Issues in Dynamic Design 1: Charge Leakage

 Dynamic logic only for fast logic to reduce leakage.




Leakage sources

 


Dominant component is subthreshold current

Solution to Charge Leakage

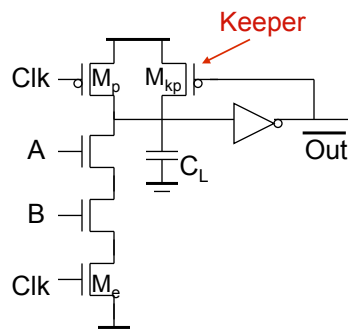


Same approach as level restorer for pass-transistor logic

Dynamic Gate VTC

 

Issues in Dynamic Design 2: Charge Sharing

 - Charge initially stored on C_L
 - C_A previously discharged




- When A rises, this charge is redistributed (shared) between C_L and C_A
- Makes Out drop below V_{DD}

EECS141

Lecture #18

13

Charge Sharing Example

 


EECS141

Lecture #18

14

Charge Sharing

 

- Two cases:
 - M_a stays on – complete charge share
 - M_a turns off – incomplete charge share

- Complete charge share:

- $Q_{Ca} = V_{Out} C_a$
 - $\Delta Q_{CL} = -V_{Out} C_a$

$$\rightarrow \Delta V_{Out} = -V_{DD} C_a / (C_a + C_L)$$

- Incomplete charge share:

- $Q_{Ca} = (V_{DD} - V_{TN}^*) C_a$
 - $\Delta Q_{CL} = -(V_{DD} - V_{TN}^*) C_a$


$$\rightarrow \Delta V_{Out} = -(V_{DD} - V_{TN}^*) C_a / C_L$$

EECS141

Lecture #18

15

Solution to Charge Sharing

 


- Keeper helps a lot
 - Can still get failures if Out drops below inverter V_{sw}
- Another option: precharge internal nodes
 - Increases power and area

EECS141

Lecture #18

16

 Issues in Dynamic Design 3: Clock Feedthrough





Coupling between Out and Clk input of the precharge device due to the gate to drain capacitance. So voltage of Out can rise above V_{DD} . The fast rising (and falling edges) of the clock **couple** to Out.

EECS141

Lecture #18

17

Clock Feedthrough

  


EECS141

Lecture #18

18

Issues in Dynamic Design 4: Backgate Coupling

 


EECS141

Lecture #18

19

Backgate Coupling Effect

 

EECS141

Lecture #18

20


Other Effects

- ❑ Capacitive coupling
- ❑ Substrate coupling
- ❑ Minority charge injection
- ❑ Supply noise (ground bounce)




Domino Logic

Cascading Dynamic Gates

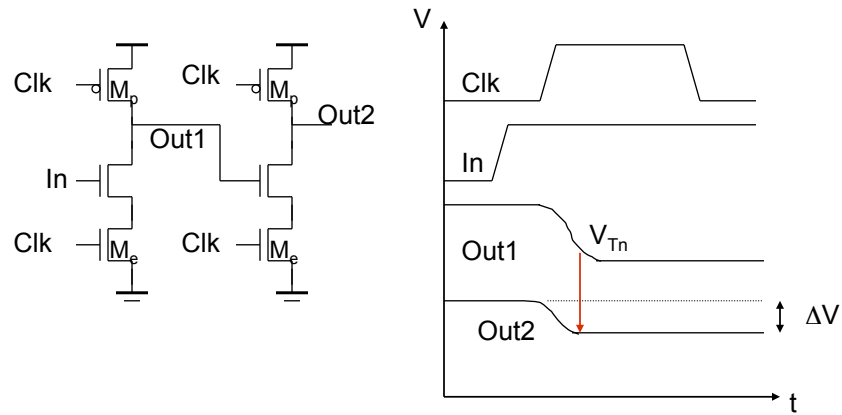


Only 0 → 1 transitions allowed at inputs!

Domino Logic

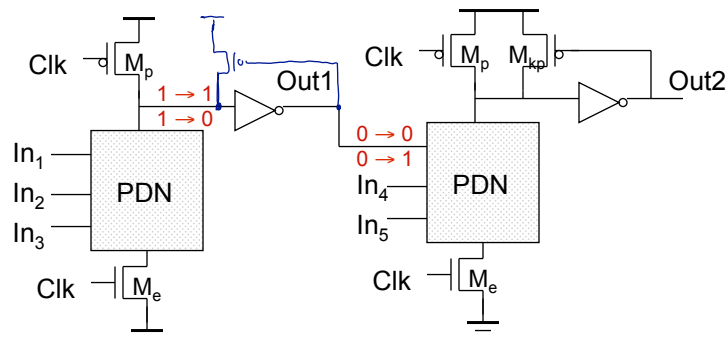

Why Named Domino?

 

Like falling dominos!

EECS141

Lecture #18

25

Properties of Domino Logic


- Only non-inverting logic can be implemented
- Very high speed
 - static inverter can be skewed, only L-H transition critical
 - Input capacitance reduced – smaller logical effort

EECS141


Lecture #18

26

Domino Logic LE

 
 
$$\begin{aligned} LE_{dyn} &= \\ LE_{inv} &= 1 \\ \pi LE &= \end{aligned}$$




$$\begin{aligned} LE_{dyn} &= \\ LE_{inv} &= 1 \\ \pi LE &= \end{aligned} \quad LE_{static} = \frac{7}{3}$$

EECS141

Lecture #18


27

Domino Logic LE (skewed static gate)

 

$$\begin{aligned} LE_{dyn} &= \\ LE_{inv} &= \\ \pi LE &= \end{aligned}$$

reference inverter:

 


EECS141

Lecture #18

28

Buffer “Average” LE

Dominio buffer:

 

$$LE_{div} = \frac{2}{3}$$

$$LE_{sinu} = \frac{5}{6}$$

$$\pi LE = \frac{10}{18}$$


"Average" $LE = \sqrt{10/18} \approx \frac{3}{4}$

EECS141

Lecture #18

29

Designing with Domino Logic

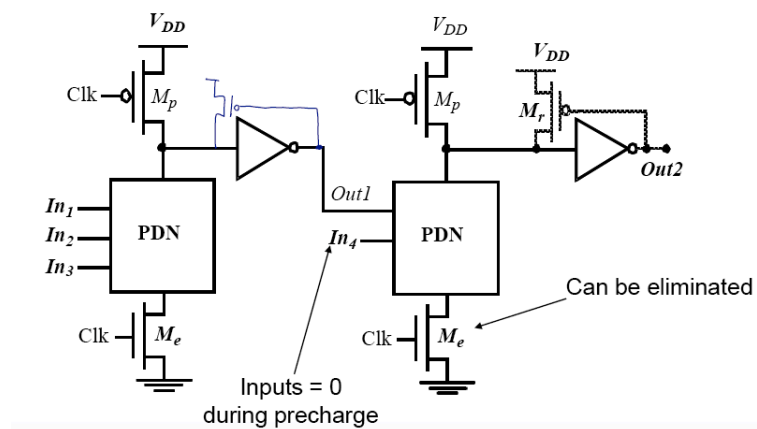

EECS141

Lecture #18

30




CMOS Layout

EECS141

Lecture #18

31

Complex CMOS Gate

 

EECS141

Lecture #18

32

Cell Design

□ Standard Cells

- General purpose logic
- Used to synthesize RTL/HDL
- Same height, varying width

□ Datapath Cells


- For regular, structured designs (arithmetic)
- Includes some wiring in the cell

EECS141

Lecture #18

33

Standard Cell Methodology

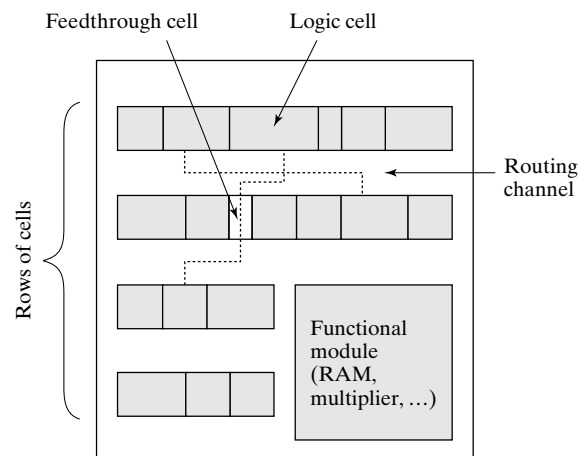


EECS141


Lecture #18

34

Standard Cells – Then and Now

 

(a)

 


(b)

EECS141

Lecture #18

35

Standard Cell Layout Methodology

 


EECS141

Lecture #18

36

Standard Cells

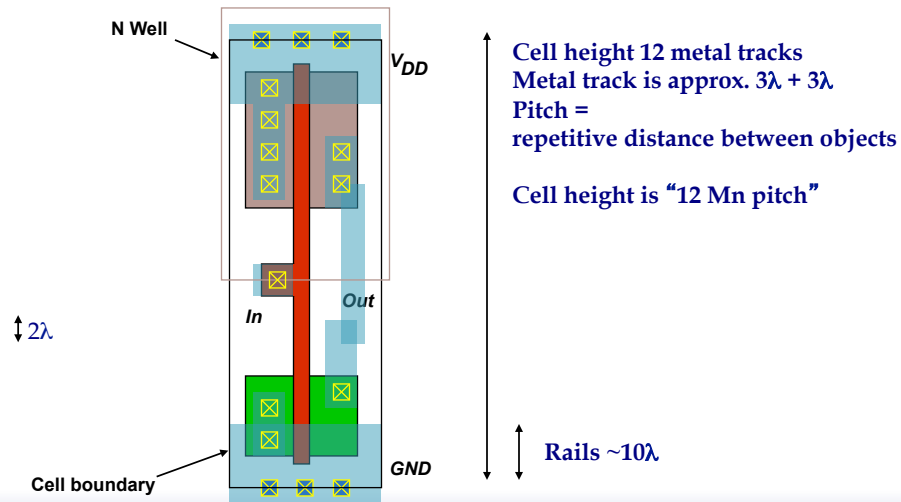


EECS141

Lecture #18

37

Standard Cells

 


EECS141


Lecture #18

38

Standard Cells

 

2-input NAND gate

 



EECS141

Lecture #18

39

Stick Diagrams

Contains no dimensions
Represents relative positions of transistors

  


EECS141

Lecture #18

40

Two Versions of $C \cdot (A + B)$

 


EECS141

Lecture #18

41

Logic Graphs

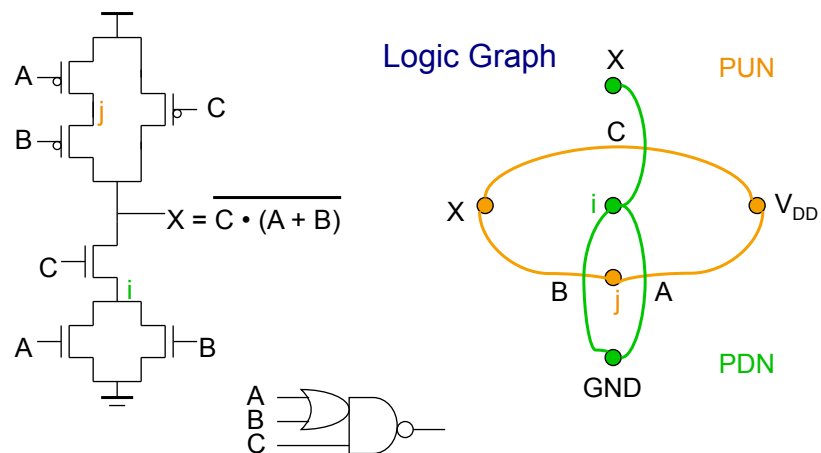

EECS141

Lecture #18

42


Consistent Euler Path

A B C

Has PDN and PUN

B C A

Has PUN, but no PDN


 


EECS141

Lecture #18

43

OAI22 Logic Graph

  


EECS141


Lecture #18

44


Example: $x = ab + cd$

 

 (a) Logic graphs for $\overline{(ab+cd)}$



(b) Euler Paths $\{a b c d\}$

 

(c) stick diagram for ordering $\{a b c d\}$


EECS141

Lecture #18


45

Multi-Fingered Transistors

One finger

 

Two fingers (folded)

 

Less diffusion capacitance

EECS141

Lecture #18

46