



EE141-Spring 2012 Digital Integrated Circuits

Lecture 23 Clocks + Power

EECS141

Lecture #23

1

Administrativa

- ❑ Project Phase 2 due Today.
- ❑ Project Phase 3 to be launched today
- ❑ Assignment 9 posted today
 - One more assignment (#10) – will not be graded

EECS141

Lecture #23

2

Class Material

- Last lecture
 - Registers + Timing
- Today's lecture
 - Timing + Clocks
- Reading (Ch 10)




Clock Distribution

Clock Distribution

- Single clock generally used to synchronize all logic on the same chip
 - Need to distribute clock over the entire die
 - While maintaining low skew/jitter
 - (And without burning too much power)


What matters is to minimize clock skew – not clock delay

H-Tree

 

Equal wire length/number of buffers to get to every location

Clock Grid

 


- No RC matching
- But huge power

EECS141


Lecture #23

7

Example: DEC Alpha 21164 (1995)

 

Clock waveform

 


Location of clock driver on die

- 2 phase single wire clock, distributed globally
- 2 distributed driver channels
 - Reduced RC delay/skew
 - Improved thermal distribution
 - 3.75nF clock load, 20W power
 - 58 cm final driver width
- Local inverters for latching
- Conditional clocks in caches to reduce power
- More complex race checking
- Device variation


EECS141

Lecture #23



8

 

Clock Skew in Alpha Processor

 

  EV6 (Alpha 21264) Clocking 600 MHz – 0.35 micron CMOS




- 2 Phase, with multiple conditional buffered clocks
 - 2.8 nF clock load
 - 40 cm final driver width
- Local clocks can be gated “off” to save power
- Reduced load/skew
- Reduced thermal issues
- Multiple clocks complicate race checking

EECS141

Lecture #23

11

21264 Clocking

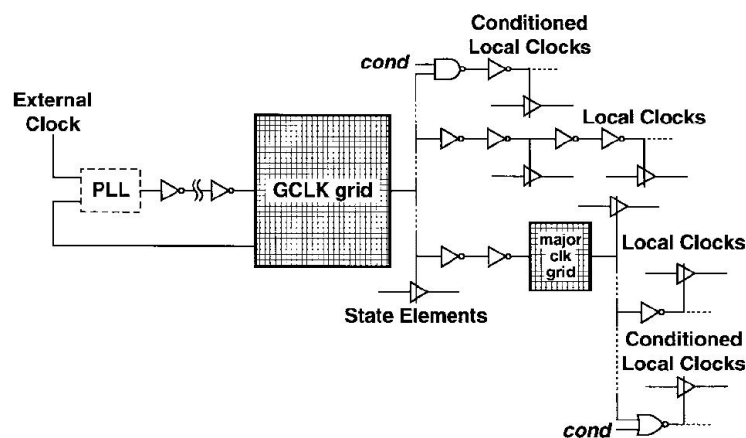


EECS141

Lecture #23

12¹²

EV6 Clock Results

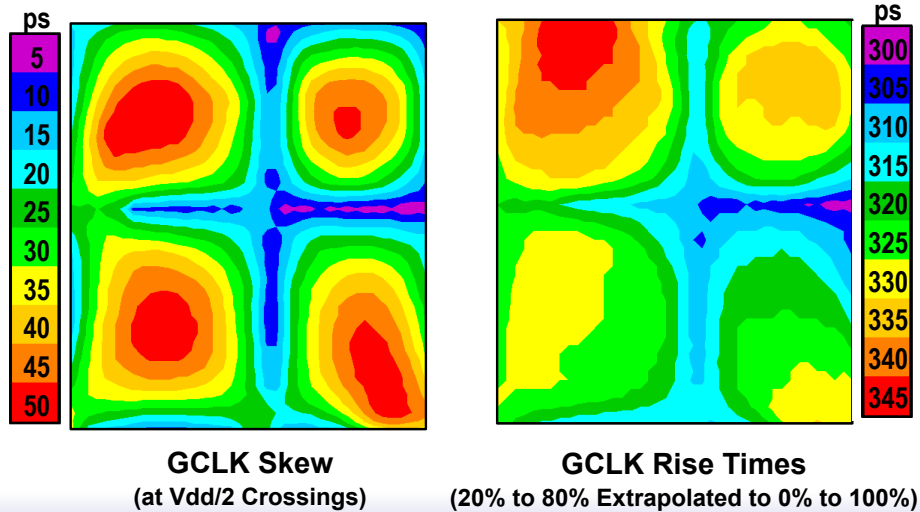


EECS141

Lecture #23

13

EV7 Clock Hierarchy (2002)

 Active Skew Management and Multiple Clock Domains



- + widely dispersed drivers
- + DLLs compensate static and low-frequency variation
- + divides design and verification effort
- DLL design and verification is added work
- + tailored clocks

EECS141


Lecture #23

14

Clock Animations

□ By Phillip Restle (IBM)

<http://www.research.ibm.com/people/r/restle/resonate.html>

 

EECS141

Lecture #23

15



Power Distribution

EECS141


Lecture #23

16

Impact of Resistance


- ❑ We have already learned how to drive RC interconnect
- ❑ Impact of resistance is commonly seen in power supply distribution:
 - IR drop
 - Voltage variations
- ❑ Power supply is distributed to minimize the IR drop and the change in current due to switching of gates

RI Introduced Noise

 


Resistance and the Power Distribution Problem

Before

 

After

 

- Requires fast and accurate peak current prediction
- Heavily influenced by packaging technology

Source: Cadence

EECS141

Lecture #23

19

Power Distribution


- ❑ Low-level distribution is in Metal 1
- ❑ Power has to be 'strapped' in higher layers of metal.
- ❑ The spacing is set by IR drop, electromigration, inductive effects
- ❑ Always use multiple contacts on straps

EECS141

Lecture #23

20

Power and Ground Distribution

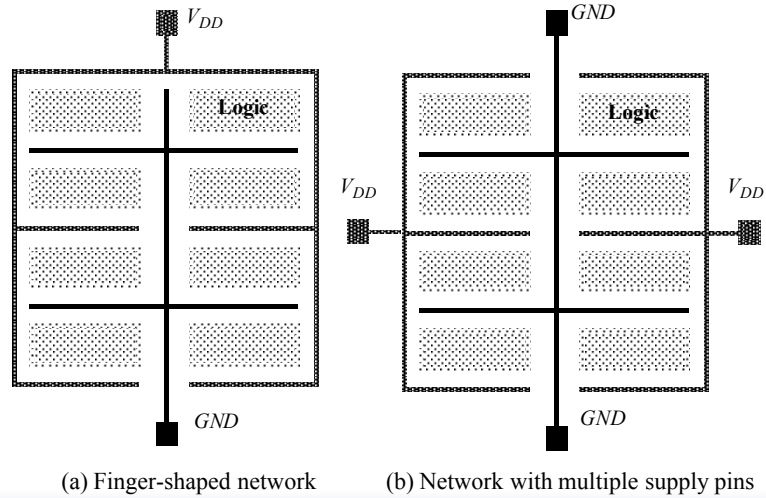

EECS141

Lecture #23

21


3 Metal Layer Approach (EV4)

3rd “coarse and thick” metal layer added to the technology for EV4 design

Power supplied from two sides of the die via 3rd metal layer

2nd metal layer used to form power grid

90% of 3rd metal layer used for power/clock routing

 

EECS141

Courtesy HP
Lecture #23

22


4 Metal Layers Approach (EV5)

4th “coarse and thick” metal layer added to the technology for EV5 design

Power supplied from four sides of the die

Grid strapping done all in coarse metal

90% of 3rd and 4th metals used for power/clock routing

 

EECS141

Courtesy HP
Lecture #23

23


6 Metal Layer Approach – EV6

2 reference plane metal layers added to the technology for EV6 design

Solid planes dedicated to Vdd/Vss

Significantly lowers resistance of grid

Lowers on-chip inductance

 


EECS141

Courtesy HP
Lecture #23

²⁴
24

Electromigration (1)

 


Limits dc-current to 1 mA/ μm

EECS141

Lecture #23

25

Electromigration (2)

 

EECS141

Lecture #23

26

CMOS Transistor Scaling



EECS141

Lecture #23

27

Goals of Technology Scaling

- ❑ Make things cheaper:
 - Want to sell more functions (transistors) per chip for the same money
 - Or build same products cheaper
 - Price of a transistor has to be reduced
- ❑ But also want to be faster, smaller, lower power...

EECS141

Lecture #23

28

Technology Scaling

- ❑ Benefits of 30% “Dennard” scaling (1974):
 - Double transistor density
 - Reduce gate delay by 30% (increase operating frequency by 43%)
 - Reduce energy per transition by 65% (50% power savings @ 43% increase in frequency)
- ❑ Die size used to increase by 14% per generation (not any more)
- ❑ Technology generation spans 2-3 years

EECS141

Lecture #23

29

Moore was not always accurate

Projected 2000 Wafer, circa 1975




EECS141

Lecture #23


30

Technology Scaling (1)

 


Minimum Feature Size

Technology Scaling (2)

 

Number of components per chip

Technology Scaling (3)

 


Propagation Delay

EECS141


Lecture #23

33

Technology Scaling (4)

 

(a) Power dissipation vs. year.

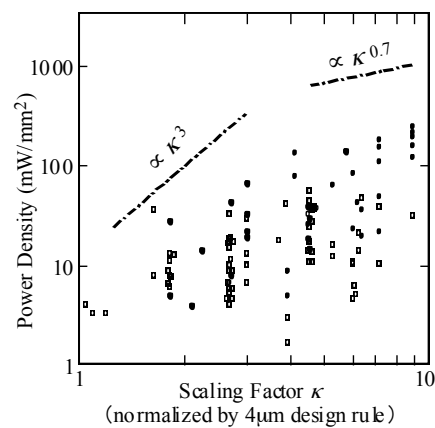

(b) Power density vs. scaling factor.

From Kuroda

EECS141

Lecture #23

34

Technology Scaling Models

- **Full Scaling (Constant Electrical Field)**

ideal model — dimensions and voltages scale together by the same factor S

- **Fixed Voltage Scaling**

most common model until 1990's
only dimensions scale, voltages remain constant

- **General Scaling**


most realistic for today's situation —
voltages and dimensions scale with different factors

EECS141

Lecture #23

35

Scaling

 

EECS141

Lecture #23

36

Full Scaling (Dennard, Long-Channel)

- $W, L, t_{ox}: 1/S$
- $V_{DD}, V_T: 1/S$
- Area: WL
- $C_{ox}: 1/t_{ox}$
- $C_L: C_{ox}WL$
- $I_D: C_{ox}(W/L)(V_{DD}-V_T)^2$
- $R_{eq}: V_{DD}/I_{DSAT}$

EECS141

Lecture #23

37

Full Scaling (Dennard, Long-Channel)

- $W, L, t_{ox}: 1/S$
- $V_{DD}, V_T: 1/S$
- $t_p: R_{eq}C_L$
- $P_{avg}: C_L V_{DD}^2/t_p$
- $P_{avg}/A: C_{ox} V_{DD}^2/t_p$

EECS141

Lecture #23

38

Scaling Relationships for Long Channel Devices

| Parameter | Relation | Full Scaling | General Scaling | Fixed Voltage Scaling |
|-------------------|------------------|--------------|-----------------|-----------------------|
| W, L, t_{ox} | | $1/S$ | $1/S$ | $1/S$ |
| V_{DD}, V_T | | $1/S$ | $1/U$ | 1 |
| N_{SUB} | V/W_{depl}^2 | S | S^2/U | S^2 |
| Area/Device | WL | $1/S^2$ | $1/S^2$ | $1/S^2$ |
| C_{ox} | $1/t_{ox}$ | S | S | S |
| C_L | $C_{ox}WL$ | $1/S$ | $1/S$ | $1/S$ |
| k_n, k_p | $C_{ox}W/L$ | S | S | S |
| I_{av} | $k_{n,p} V^2$ | $1/S$ | S/U^2 | S |
| t_p (intrinsic) | $C_L V / I_{av}$ | $1/S$ | U/S^2 | $1/S^2$ |
| P_{av} | $C_L V^2 / t_p$ | $1/S^2$ | S/U^3 | S |
| PDP | $C_L V^2$ | $1/S^3$ | $1/SU^2$ | $1/S$ |

EECS141

Lecture #23

39

Full Scaling (Dennard, Short-Channel)

- W, L, t_{ox} : $1/S$
- V_{DD}, V_T : $1/S$
- Area: WL
- C_{ox} : $1/t_{ox}$
- C_L : $C_{ox}WL$
- I_D : $WC_{ox}V_{sat}(V_{DD}-V_T-V_{SAT}/2)$
- R_{eq} : V_{DD}/I_{DSAT}

EECS141

Lecture #23

40

Full Scaling (Dennard, Short-Channel)

- W, L, t_{ox} : $1/S$
- V_{DD}, V_T : $1/S$
- t_p : $R_{eq} C_L$
- P_{avg} : $C_L V_{DD}^2 / t_p$
- P_{avg}/A : $C_{ox} V_{DD}^2 / t_p$

EECS141

Lecture #23

41

Transistor Scaling (Velocity-Saturated Devices)

| Parameter | Relation | Full Scaling | General Scaling | Fixed-Voltage Scaling |
|-----------------|------------------|--------------|-----------------|-----------------------|
| W, L, t_{ox} | | $1/S$ | $1/S$ | $1/S$ |
| V_{DD}, V_T | | $1/S$ | $1/U$ | 1 |
| N_{SUB} | V/W_{depl}^2 | S | S^2/U | S^2 |
| Area/Device | WL | $1/S^2$ | $1/S^2$ | $1/S^2$ |
| C_{ox} | $1/t_{ox}$ | S | S | S |
| C_{gate} | $C_{ox}WL$ | $1/S$ | $1/S$ | $1/S$ |
| k_n, k_p | $C_{ox}W/L$ | S | S | S |
| I_{sat} | $C_{ox}VV$ | $1/S$ | $1/U$ | 1 |
| Current Density | $I_{sat}/Area$ | S | S^2/U | S^2 |
| R_{on} | V/I_{sat} | 1 | 1 | 1 |
| Intrinsic Delay | $R_{on}C_{gate}$ | $1/S$ | $1/S$ | $1/S$ |
| P | $I_{sat}V$ | $1/S^2$ | $1/U^2$ | 1 |
| Power Density | $P/Area$ | 1 | S^2/U^2 | S^2 |

EECS141

Lecture #23

42

An interesting question

□ What ~~will~~ did cause this model to break?

- Leakage set by kT/q
 - Temp. does not scale
 - V_T set to minimize power
- Power actually increased
 - Leakage increased drastically
 - f increased faster than device speed
 - Hit cooling limit
- Process Variation
 - Hard to build very small things accurately (less averaging)

Wire Scaling