



EE141-Spring 2012 Digital Integrated Circuits

Lecture 24 Scaling + Energy

EECS141

Lecture #24

1

Administrativa

- ❑ Project Phase 2 due Today.
- ❑ Project Phase 3 to be launched today
- ❑ Assignment 9 posted today
 - One more assignment (#10) – will not be graded

EECS141

Lecture #24

2

CMOS Scaling



EECS141

Lecture #24

3

Technology Scaling

- ❑ Benefits of 30% “Dennard” scaling (1974):
 - Double transistor density
 - Reduce gate delay by 30% (increase operating frequency by 43%)
 - Reduce energy per transition by 65% (50% power savings @ 43% increase in frequency)
- ❑ Die size used to increase by 14% per generation (not any more)
- ❑ Technology generation spans 2-3 years

EECS141

Lecture #24

4

Full Scaling (Dennard, Long-Channel)

- $W, L, t_{ox}: 1/S$
- $V_{DD}, V_T: 1/S$
- Area: WL
- $C_{ox}: 1/t_{ox}$
- $C_L: C_{ox}WL$
- $I_D: C_{ox}(W/L)(V_{DD}-V_T)^2$
- $R_{eq}: V_{DD}/I_{DSAT}$

EECS141

Lecture #24

5

Full Scaling (Dennard, Long-Channel)

- $W, L, t_{ox}: 1/S$
- $V_{DD}, V_T: 1/S$
- $t_p: R_{eq}C_L$
- $P_{avg}: C_L V_{DD}^2/t_p$
- $P_{avg}/A: C_{ox} V_{DD}^2/t_p$

EECS141

Lecture #24

6

Scaling Relationships for Long Channel Devices

Parameter	Relation	Full Scaling	General Scaling	Fixed Voltage Scaling
W, L, t_{ox}		$1/S$	$1/S$	$1/S$
V_{DD}, V_T		$1/S$	$1/U$	1
N_{SUB}	V/W_{depl}^2	S	S^2/U	S^2
Area/Device	WL	$1/S^2$	$1/S^2$	$1/S^2$
C_{ox}	$1/t_{ox}$	S	S	S
C_L	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
k_n, k_p	$C_{ox}W/L$	S	S	S
I_{av}	$k_{n,p} V^2$	$1/S$	S/U^2	S
t_p (intrinsic)	$C_L V / I_{av}$	$1/S$	U/S^2	$1/S^2$
P_{av}	$C_L V^2 / t_p$	$1/S^2$	S/U^3	S
PDP	$C_L V^2$	$1/S^3$	$1/SU^2$	$1/S$

EECS141

Lecture #24

7

Full Scaling (Dennard, Short-Channel)

- W, L, t_{ox} : $1/S$
- V_{DD}, V_T : $1/S$
- Area: WL
- C_{ox} : $1/t_{ox}$
- C_L : $C_{ox}WL$
- I_D : $WC_{ox}v_{sat}(V_{DD}-V_T-V_{SAT}/2)$
- R_{eq} : V_{DD}/I_{DSAT}

EECS141

Lecture #24

8

Full Scaling (Dennard, Short-Channel)

- W, L, t_{ox} : $1/S$
- V_{DD}, V_T : $1/S$
- t_p : $R_{eq} C_L$
- P_{avg} : $C_L V_{DD}^2 / t_p$
- P_{avg}/A : $C_{ox} V_{DD}^2 / t_p$

EECS141

Lecture #24

9

Transistor Scaling (Velocity-Saturated Devices)

Parameter	Relation	Full Scaling	General Scaling	Fixed-Voltage Scaling
W, L, t_{ox}		$1/S$	$1/S$	$1/S$
V_{DD}, V_T		$1/S$	$1/U$	1
N_{SUB}	V/W_{depl}^2	S	S^2/U	S^2
Area/Device	WL	$1/S^2$	$1/S^2$	$1/S^2$
C_{ox}	$1/t_{ox}$	S	S	S
C_{gate}	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
k_n, k_p	$C_{ox}W/L$	S	S	S
I_{sat}	$C_{ox}VV$	$1/S$	$1/U$	1
Current Density	$I_{sat}/Area$	S	S^2/U	S^2
R_{on}	V/I_{sat}	1	1	1
Intrinsic Delay	$R_{on}C_{gate}$	$1/S$	$1/S$	$1/S$
P	$I_{sat}V$	$1/S^2$	$1/U^2$	1
Power Density	$P/Area$	1	S^2/U^2	S^2

EECS141

Lecture #24

10

Interesting questions


□ What causes this model to break down?

- Leakage set by kT/q
 - Temp. does not scale
 - V_T set to minimize power
- Power actually increased
 - Leakage increased drastically
 - f increased faster than device speed
 - Hit cooling limit
- Process Variation
 - Hard to build very small things accurately (less averaging)

Scaling Assumptions


Technology (High Volume)	45nm (2008)	32nm (2010)	22nm (2012)	16nm (2014)	11nm (2016)	8nm (2018)	5nm (2020)
Transistor density	1.75	1.75	1.75	1.75	1.75	1.75	1.75
Frequency scaling	15%	10%	8%	5%	4%	3%	2%
Vdd scaling	-10%	-7.5%	-5%	-2.5%	-1.5%	-1%	-0.5%
Dimension & Capacitance	0.75	0.75	0.75	0.75	0.75	0.75	0.75
SD Leakage scaling/micron	1X Optimistic to 1.43X Pessimistic						

45nm Core + Local Memory

 

6mm², 3.5GHz, 7GF, 1.2W

8nm Core + Local Memory

 


~0.6mm

0.34mm², 4.6GHz, 9.2GF, 0.24 to 0.46W


Courtesy; S. Borkar, Intel

Performance Roadmap

 

13

From Giga to Exa, via Tera & Peta

 

14

Wire Scaling

□ Wire scaling model

- $C = WL/t_{ox}$
- $R = \rho L/(WH)$
- $t_p = 0.38RC$
- $E = C V_{DD}^2$



Energy/Power Revisited

Transition Activity and Power

□ Energy consumed in N cycles, E_N :

$$E_N = C_L \cdot V_{DD}^2 \cdot n_{0 \rightarrow 1}$$

$n_{0 \rightarrow 1}$ – number of $0 \rightarrow 1$ transitions in N cycles

$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f = \left(\lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \right) \cdot C_L \cdot V_{DD}^2 \cdot f$$

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \cdot f$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f$$

EECS141

Lecture #24

17

Factors Affecting Transition Activity

- “Static” component (does not account for timing)
 - Type of Logic Function (NOR vs. XOR)
 - Type of Logic Style (Static vs. Dynamic)
 - Signal Statistics
 - Inter-signal Correlations
- “Dynamic” or timing dependent component
 - Circuit Topology
 - Signal Statistics and Correlations

EECS141

Lecture #24

18

Type of Logic Function: NOR

Example: Static 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume **signal probabilities**

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then **transition probability**


$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

$$= 3/4 \times 1/4 = 3/16$$

If inputs switch every cycle

$$\alpha_{0 \rightarrow 1} = 3/16$$

Power Consumption of Dynamic Gates

 

Power only dissipated when previous Out = 0

Dynamic Power Consumption is Data Dependent

Dynamic 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume **signal probabilities**

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

Then **transition probability**


$$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$$

$$= 3/4 \times 1 = 3/4$$

Switching activity always **higher** in dynamic gates!

$$P_{0 \rightarrow 1} = P_{\text{out}=0}$$


Problem: Reconvergent Fanout

 

$$P(Z = 1) = P(B = 1) \cdot P(X = 1 \mid B=1)$$

Becomes complex and intractable fast


Inter-Signal Correlations

 

 (a) Logic circuit without reconvergent fan-out

Logic without
reconvergent fanout

$$p_{0 \rightarrow 1} = (1 - p_{\bar{A}} p_B) p_{\bar{A}} p_B$$



(b) Logic circuit with reconvergent fan-out

Logic with
reconvergent fanout

$$P(Z = 1) = p(C=1 \mid B=1) p(B=1)$$

$$p_{0 \rightarrow 1} = 0$$


- ❑ Need to use conditional probabilities to model inter-signal correlations
- ❑ CAD tools best for performing such analysis

EECS141

Lecture #24

23

Glitching in Static CMOS

 

Also known as
dynamic hazards


The result is correct,
but there is extra power dissipated

EECS141

Lecture #24

24

Example: Chain of NAND Gates

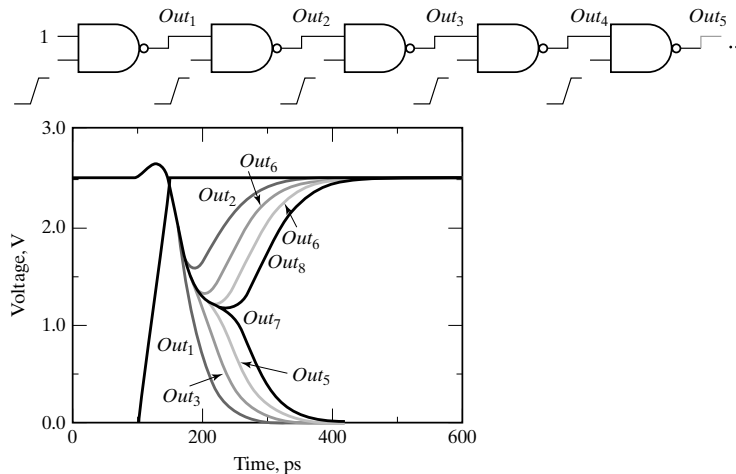

EECS141

Lecture #24

25

Principles for Power Reduction

- Most important idea: reduce waste
- Examples:
 - Don't switch capacitors you don't need to
 - Clock gating, glitch elimination, logic re-structuring
 - Don't run circuits faster than needed
 - Power $\propto V_{DD}^2$ – can save a lot by reducing supply for circuits that don't need to be as fast
 - Parallelism falls into this category
- Let's say we do a good job of that – then what?

EECS141

Lecture #24


26

Standby Power - Was Not A Concern In Earlier Days

Pentium-1: 15 Watt (5V - 66MHz)

Pentium-2: 8 Watt (3.3V- 133 MHz)

Processor in idle mode!

 


Floating Point Unit and Cache powered down when not in use

EECS141

Lecture #24

27

Energy – Performance Space

 


- Plot all possible designs on a 2-D plane
 - No matter what you do, can never get below/to the right of the solid line
- This line is called “Pareto Optimal Curve”
 - Usually (always) follows law of diminishing returns

EECS141

Lecture #24

28

Optimization Perspective

 


- Instead of metrics like EDP, this curve often provides information more directly
 - Ex1: What is minimum energy for XX performance?
 - Ex2: Over what range of performance is a new technique (dotted line) actually beneficial?

EECS141


Lecture #24

29


Expanding the Playing Field

 

Removing inefficiencies (1)

 

Alternative topologies (2)

 

Discrete options (3)

Architecture and system transformations and optimizations reshape the E-D curves

EECS141

Lecture #24

30


Reducing the Supply Voltage

(while maintaining performance)

Concurrency:

trading off clock frequency versus area to reduce power

Consider the following reference design

 

$$P_{ref} = C_{ref} \cdot V_{dd,ref}^2 \cdot f_{ref}$$

R: register,
F1, F2: combinational logic blocks
(adders, ALUs, etc)

C_{ref} : average switching capacitance


[A. Chandrakasan, JSSC'92]

EECS141

Lecture #24

31

A Parallel Implementation

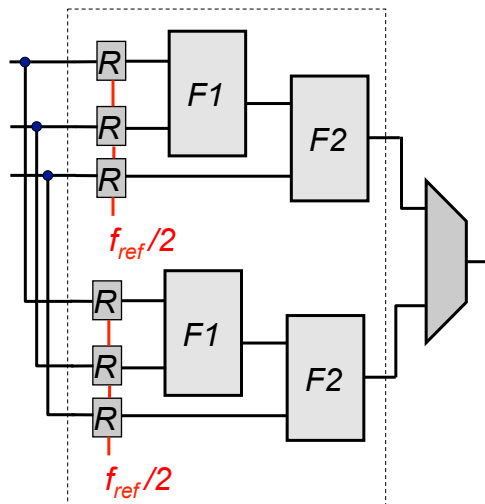

$$\begin{aligned} f_{par} &= f_{ref}/2 \\ C_{par} &= (2 + ov_{par}) \cdot C_{ref} \\ V_{dd,par} &= \epsilon_{par} \cdot V_{dd,ref} \end{aligned}$$

Almost cancels

$$P_{par} = \epsilon_{par}^2 \cdot \left(\frac{2 + ov_{par}}{2} \right) \cdot P_{ref}$$

Running slower reduces required supply voltage


Yields quadratic reduction in power

EECS141

Lecture #24

32

Example: 90nm Technology

 

Assuming
 $ov_{par} = 7.5\%$

$$P_{par} = 0.66^2 \cdot \frac{2.15}{2} \cdot P_{ref} = 0.47P_{ref}$$


$$P_{par4} = 0.52^2 \cdot \frac{4.3}{4} \cdot P_{ref} = 0.29P_{ref}$$

EECS141

Lecture #24

33

A Pipelined Implementation

 

$$\begin{aligned} f_{pipe} &= f_{ref} \\ C_{pipe} &= (1 + ov_{pipe}) \cdot C_{ref} \\ V_{dd,pipe} &= \epsilon_{pipe} \cdot V_{dd,ref} \end{aligned}$$

$$P_{pipe} = \epsilon_{pipe}^2 \cdot (1 + ov_{pipe}) \cdot P_{ref}$$

Shallower logic reduces required supply voltage
(this example assumes equal V_{dd} for par / pipe designs)

Assuming $ov_{pipe} = 10\%$

$$P_{pipe} = 0.66^2 \cdot 1.1 \cdot P_{ref} = 0.48P_{ref}$$

$$P_{pipe4} = 0.52^2 \cdot 1.1P_{ref} = 0.29P_{ref}$$


EECS141

Lecture #24

34

Increasing use of Concurrency Saturates

- Can combine parallelism and pipelining to drive V_{DD} down
- But, close to process threshold overhead of excessive concurrency starts to dominate

 


EECS141

Assuming constant 8% overhead

Lecture #24

35

Increasing use of Concurrency Saturates

 


Only option: Reduce V_{TH} as well!
But: Must consider Leakage ...

EECS141

Lecture #24

36

Mapping into the Energy-Delay Space

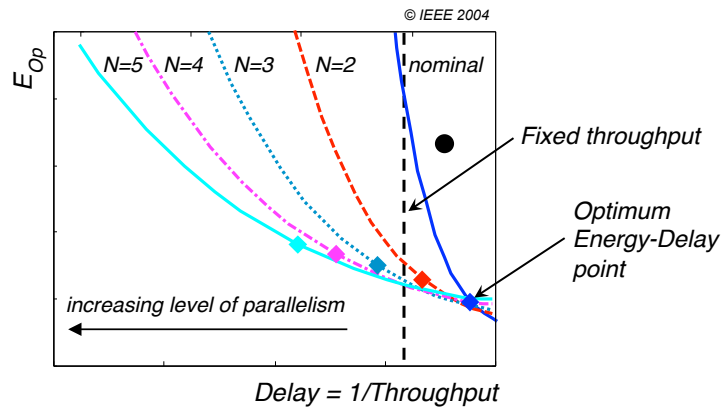

- For each level of performance, optimum amount of concurrency
- Concurrency only energy-optimal if requested throughput larger than optimal operation point of nominal function

EECS141


Lecture #24
[Ref: D. Markovic, JSSC'04]

37

What if the Required Throughput is Below Minimum?

(that is, at no concurrency)

Introduce Time-Multiplexing!

 

Absorb unused time slack by increasing clock frequency
(and voltage ...)


Again comes with some area and capacitance overhead!

EECS141

Lecture #24

38

Concurrency and Multiplexing Combined

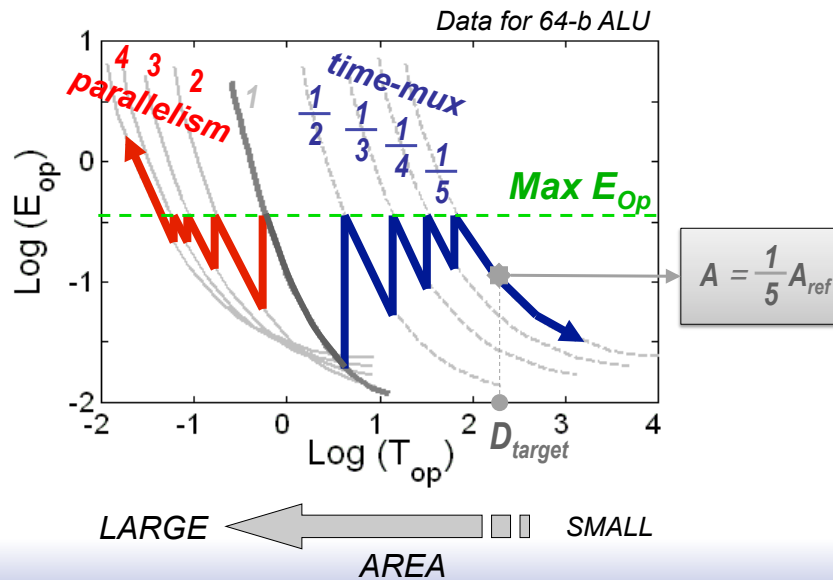

EECS141

Lecture #24

39

Some Energy-Inspired Design Guidelines

- **For maximum performance**
 - Maximize use of concurrency at the cost of area
- **For given performance**
 - Optimal amount of concurrency for minimum energy
- **For given energy**
 - Least amount of concurrency that meets performance goals
- **For minimum energy**
 - Solution with minimum overhead (that is – direct mapping between function and architecture)

EECS141

Lecture #24

40

The Leakage Challenge – Power in Standby

- ❑ With clock-gating employed in most designs, leakage power has become the dominant standby power source
- ❑ With no activity in module, leakage power should be minimized as well
 - Remember constant ratio between dynamic and static power ...
- ❑ Challenge – how to disable unit most effectively given that no ideal switches are available

EECS141

Lecture #24

41

Standby Static Power Reduction Approaches

- ❑ Transistor stacking
- ❑ Power gating
- ❑ Body biasing
- ❑ Supply voltage ramping

EECS141

Lecture #24

42

Transistor Stacking



- ❑ Off-current reduced in complex gates (see leakage power reduction @ design time)
- ❑ Some input patterns more effective than others in reducing leakage
- ❑ Effective standby power reduction strategy:
 - Select input pattern that minimizes leakage current of combinational logic module
 - Force inputs of module to correspond to that pattern during standby
- ❑ Pro's: Little overhead, fast transition
- ❑ Con: Limited effectiveness

EECS141

Lecture #24

43


Transistor Stacking

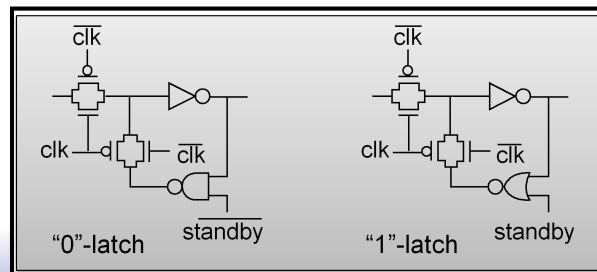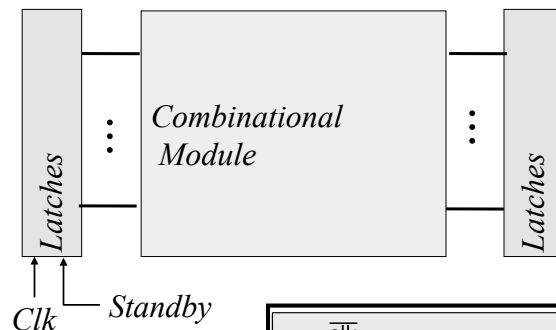


EECS141

Lecture #24
[ref: S. Narendra, ISLPED'01]

44

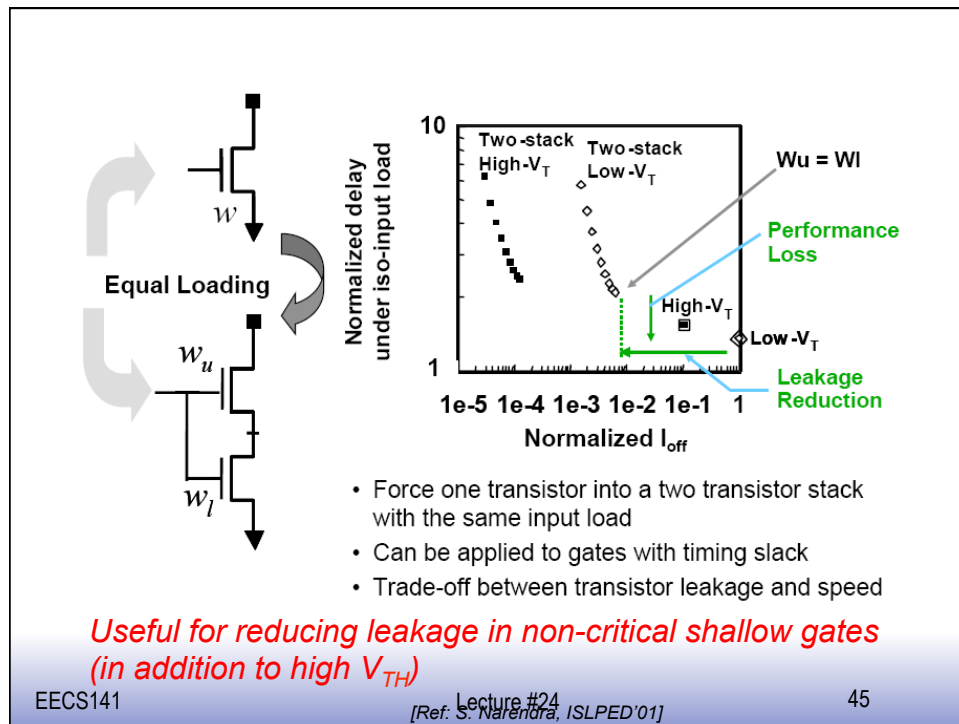

Power Gating

 


Disconnect module from supply rail(s) during standby

- Footer or header transistor, or both
- Most effective when high V_T transistors are available
- Easily introduced in standard design flows
- But ... Impact on performance


Very often called "MTCMOS" (when using high- and low- threshold devices)

Power Gating — Concept

 

Leakage current reduces because

 - Increased resistance in leakage path
- Stacking effect introduces source biasing




(similar effect at PMOS side)

EECS141

Lecture #24

47

Power Gating Options

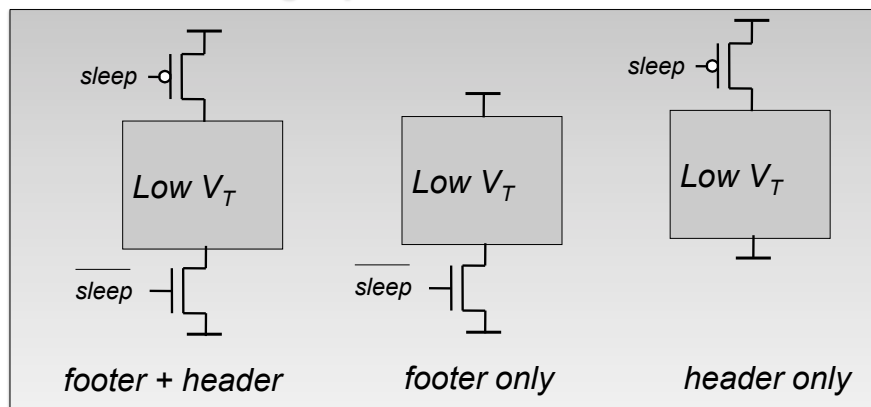

- NMOS sleeper transistor more area efficient than PMOS
- Leakage reduction more effective (under all input patterns) when both footer and header transistors are present

EECS141

Lecture #24

48