



## *EE141-Spring 2012 Digital Integrated Circuits*

### Lecture 22 Timing + Clocks

EECS141

Lecture #22

1

### *Administrativa*

- ❑ Project Phase 2 due Today.
- ❑ Project Phase 3 to be launched today
- ❑ Assignment 9 posted today
  - One more assignment (#10) – will not be graded

EECS141

Lecture #22

2


## *Class Material*

- Last lecture
  - Registers
- Today's lecture
  - Timing
- Reading (Ch 10)



## *Timing*

## Synchronous Timing

 


EECS141

Lecture #16

5

## Latch Parameters

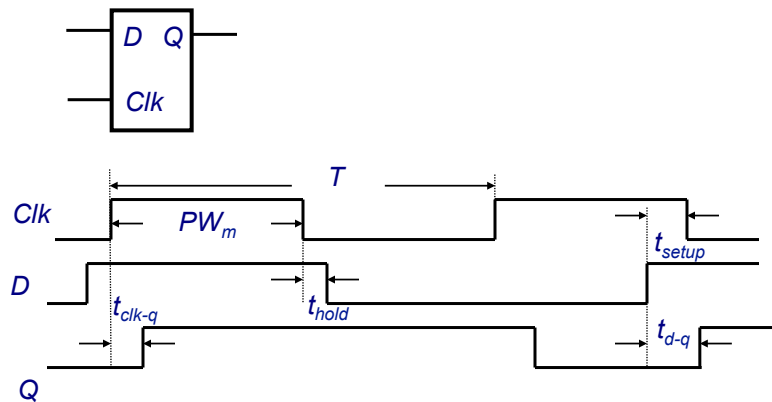


*Delays can be different for rising and falling data transitions*

EECS141

Lecture #16

6

## Register Parameters

 


*Delays can be different for rising and falling data transitions*

EECS141

Lecture #16

7

## Timing Constraints

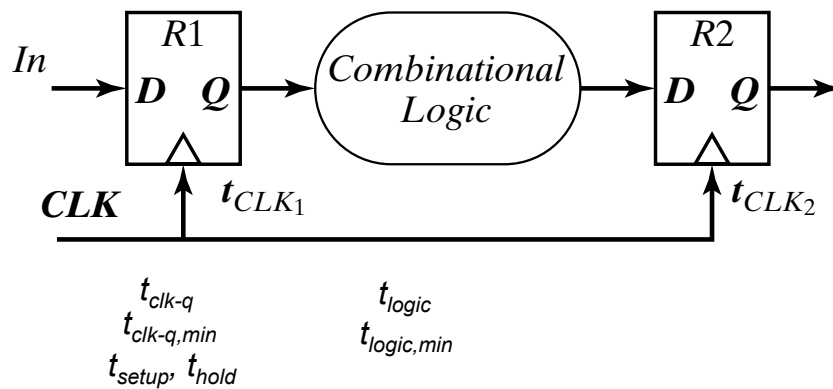


EECS141

Lecture #16

8

## Timing Constraints

 

Cycle time (max):  $T_{Clk} > t_{clk-q} + t_{logic} + t_{setup}$

Race margin (min):  $t_{hold} < t_{clk-q,min} + t_{logic,min}$

## Clock Nonidealities

### □ Clock skew

- Spatial variation in temporally equivalent clock edges; deterministic + random,  $t_{SK}$


### □ Clock jitter

- Temporal variations in consecutive edges of the clock signal; modulation + random noise
- Cycle-to-cycle (short-term)  $t_{JS}$
- Long term  $t_{JL}$

### □ Variation of the pulse width

- Important for level sensitive clocking

## Clock Uncertainties

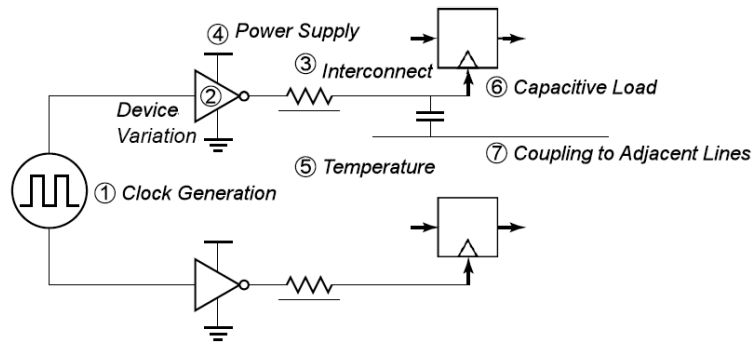


*Sources of clock uncertainty*

EECS141

Lecture #16

11

## Clock Skew and Jitter

 


- Both skew and jitter affect the effective cycle time and the race margin

EECS141

Lecture #16

12

## Clock Skew

 


EECS141


Lecture #16

13

## Positive and Negative Skew

 

(a) Positive skew

 


(b) Negative skew

EECS141

Lecture #16


14

## Positive Skew

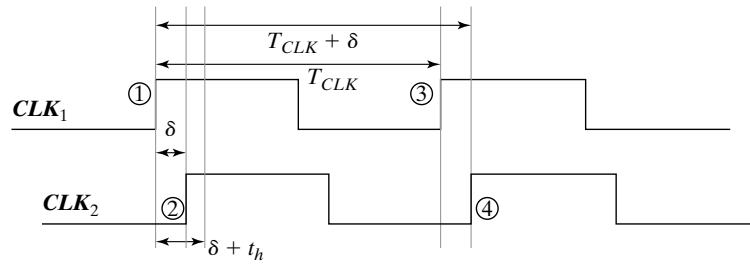

*Launching edge arrives before the receiving edge*


## Negative Skew

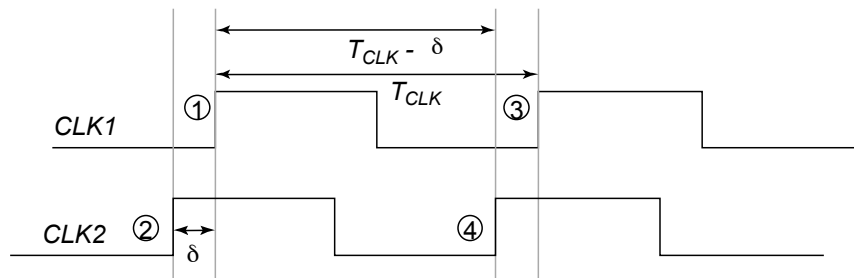

*Receiving edge arrives before the launching edge*



## Timing Constraints

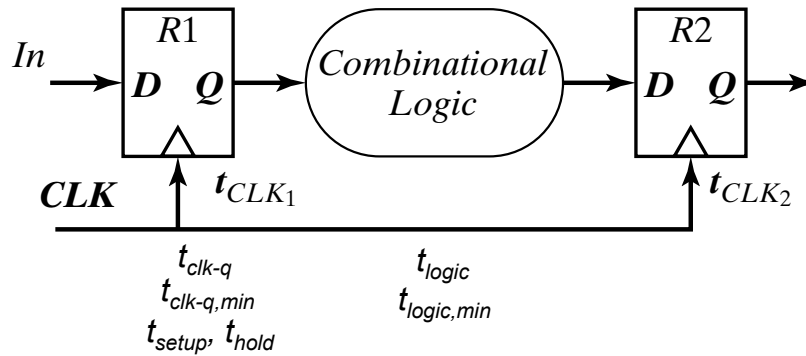

**Minimum cycle time:**

$$T_{clk} + \delta = t_{clk-q} + t_{setup} + t_{logic}$$


Worst case is when receiving edge arrives early (negative  $\delta$ )

EECS141

Lecture #16

17

## Timing Constraints

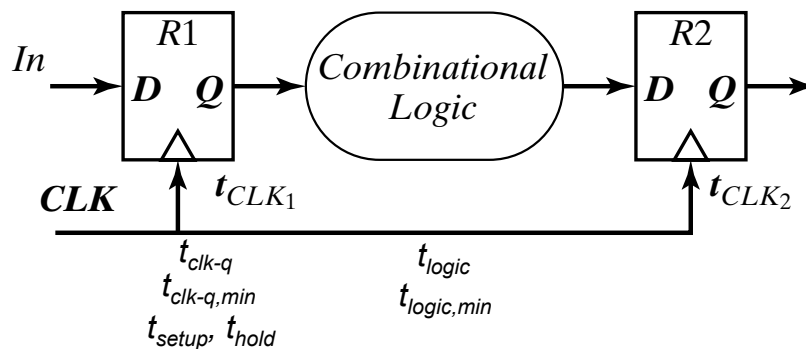

**Hold time constraint:**

$$t_{(clk-q,min)} + t_{(logic,min)} > t_{hold} + \delta$$


Worst case is when receiving edge arrives late  
Race between data and clock

EECS141

Lecture #16

18

## Longest Logic Path in Edge-Triggered Systems

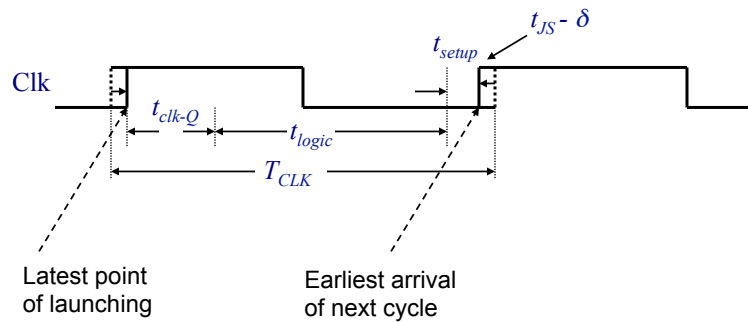

EECS141

Lecture #16

19

## Clock Constraints in Edge-Triggered Systems

If launching edge is late and receiving edge is early, the data will not be too late if:

$$t_{clk-q} + t_{logic} + t_{setup} < T_{CLK} - t_{JS,1} - t_{JS,2} + \delta$$

Minimum cycle time is determined by the maximum delays through the logic

$$t_{clk-q} + t_{logic} + t_{setup} - \delta + 2t_{JS} < T_{CLK}$$


**Skew can be either positive or negative**

EECS141

Lecture #16

20

## Shortest Path

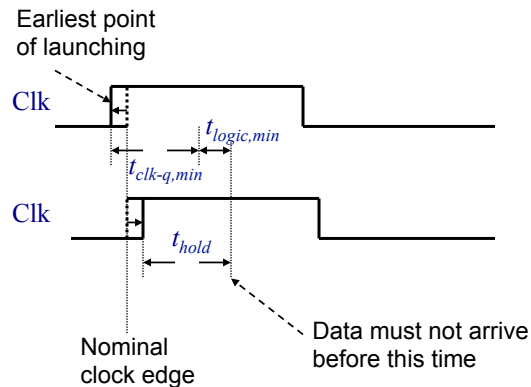

EECS141

Lecture #16

21

## Clock Constraints in Edge-Triggered Systems

If launching edge is early and receiving edge is late:

$$t_{clk-q,min} + t_{logic,min} - t_{JS,1} > t_{hold} + t_{JS,2} + \delta$$

Minimum logic delay

$$t_{clk-q,min} + t_{logic,min} > t_{hold} + 2t_{JS} + \delta$$


(This assumes jitter at launching and receiving clocks are independent – which usually is not true)

EECS141


Lecture #16

22

Datapath with Feedback

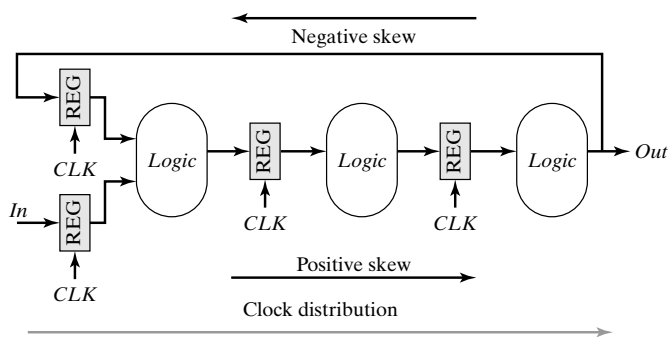

Pipelining

 


Reference

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log( a_1 + b_1 )$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log( a_2 + b_2 )$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log( a_3 + b_3 )$

Pipelined

## Latch-Based Clocking

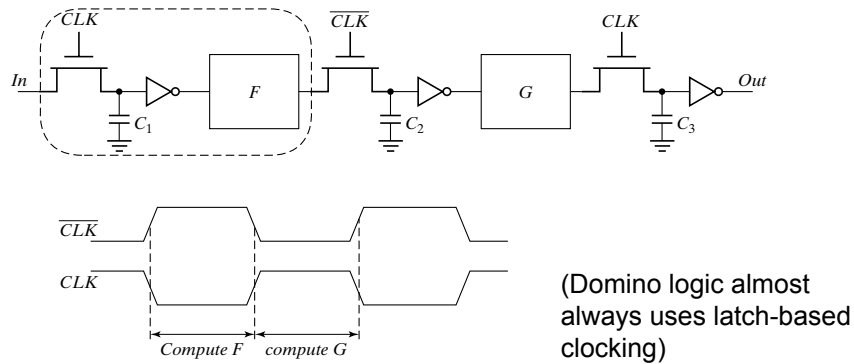

EECS141

Lecture #16

25

## Latch vs. Flip-flop

### □ In a flip-flop based system:

- Data launches on one rising edge
  - And must arrive before next rising edge
- If data arrives late, system fails
  - If it arrives early, wasting time
- Flip-flops have hard edges

### □ In a latch-based system:


- Data can pass through latch while it is transparent
- Long cycle of logic can borrow time into next cycle
  - As long as each loop finished in one cycle

EECS141

Lecture #16

26

## Time Borrowing Example

 

EECS141

Lecture #16

27

## Latch vs. Flip-flop Summary

- ❑ Flip-flops generally easier to use
  - Most digital ASICs designed with register-based timing
- ❑ But, latches (both pulsed and level-sensitive) allow more flexibility
  - And hence can potentially achieve higher performance
  - Latches can also be made more tolerant of clock uncertainty
  - More in EE241

EECS141

Lecture #16

28