



EE141-Spring 2012 Digital Integrated Circuits

Lecture 14 Memory

EECS141

Lecture #14

1


Administrativa

- ☐ ^{logic depth} Homework 6 due March 16.
- ☐ Project Phase 1 due on March 21. ^{global critical path}
- ☐ Midterm 2 on March 23!
- ☐ Prepare to get buzzed.

EECS141

Lecture #14

2

 


Registers and Memory

EECS141

Lecture #14


3

Combinational vs. Sequential Logic

 

(a) Combinational

$$\text{Output} = f(\text{In})$$

 

(b) Sequential

$$\text{Output} = f(\text{In}, \text{Previous In})$$

EECS141

Lecture #14

4

Registers versus Memory

不同的内存单元核心都是一样的，
对于总体的操作，布尔方程应该一
样。


面积变得重要
外围硬件共享
记忆单元可以
save area




Memory - Introduction

Storage Mechanisms

Static

 

Dynamic

 

会漏电:


因为需要写入, 所以需要接一个晶体管控制, 这个会造成漏电; 因为需要读取, 即接入一个输出晶体管, 因此电容的电会被消耗。

EECS141

Lecture #14

7

Semiconductor Memory Classification

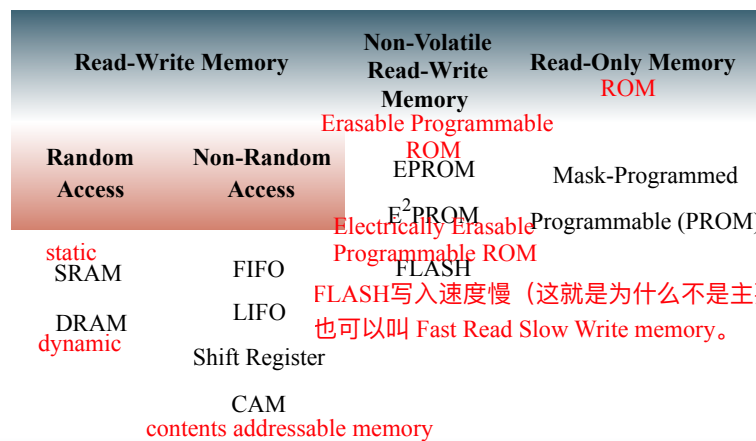

FLASH写入速度慢 (这就是为什么不是主要memory的原因) 但是读取速度快。所以也可以叫 Fast Read Slow Write memory。

EECS141

Lecture #14

8

Random Access Memories (RAM)

❑ **STATIC (SRAM)**

Data stored as long as supply is applied
Larger (6 transistors/cell)
Fast
Differential (usually)


❑ **DYNAMIC (DRAM)**

Periodic refresh required
Smaller (1-3 transistors/cell)
Slower
Single Ended



Memory - SRAM

Basic Static Memory Element

 


- If D is high, D_b will be driven low
 - Which makes D stay high


- Positive feedback

不会处于稳定态，会在0和1之间快速变换

Positive Feedback: Bi-Stability

 


Meta-Stability

 

Gain should be larger than 1 in the transition region

Writing into a Cross-Coupled Pair

 

Access transistor must be able to overpower the feedback


Writing a “1”

EECS141

Lecture #14

15

Memory Cell

 


Complementary data values are written (read) from two sides

EECS141

Lecture #14

16

6-Transistor CMOS SRAM Cell

 


EECS141

Lecture #14

17

SRAM Operation - Read

Read

 

- Q_b will get pulled up when WL first goes high
- Reading the cell should not destroy the stored value


EECS141

Lecture #14

18

在对SRAM进行写操作时，其中一条bitline置为0，另一条置为1，或者相反。
在对SRAM进行读操作时，两条bitline都要对电容进行预充电。

CMOS SRAM Analysis (Read)

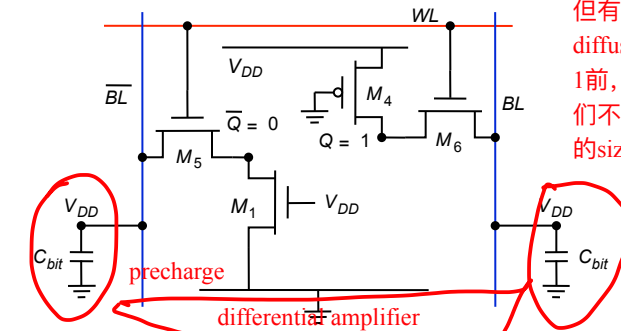

但有一个问题，当一条bitline连接的cell比较多时 diffusion capacitor的值会比较大。所以在WL变为1前，先对bitline那些电容进行预充电。这时候我们不需要再担心PMOS的size，只需要关心NMOS的size。

precharge

但是，其中一条bitline需要漫长的放电，如果我们等待它完全放完，这将会使delay很高，因此我们可以添加一个differential amplifier去比较两条bitline的电压值，然后输出VDD或者VSS！

$$k_{n,M5} \left((V_{DD} - \Delta V - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right) = k_{n,M4} \left((V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$


$$\Delta V = \frac{V_{DSATn} + CR(V_{DD} - V_{Tn}) - \sqrt{V_{DSATn}^2(1 + CR) + CR^2(V_{DD} - V_{Tn})^2}}{CR}$$

EE141

Lecture #14

19

CMOS SRAM Analysis (Read)

 


$$CR = \frac{W_1/L_1}{W_5/L_5}$$

EE141

Lecture #14

20

CMOS SRAM Analysis (Write)

 

$$k_{n,M6} \left((V_{DD} - V_{Tn}) V_Q - \frac{V_Q^2}{2} \right) = k_{p,M4} \left((V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)$$


$$V_Q = V_{DD} - V_{Tn} - \sqrt{(V_{DD} - V_{Tn})^2 - 2 \frac{\mu_p}{\mu_n} PR \left((V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)}$$

EE141

Lecture #14

21

CMOS SRAM Analysis (Write)

 


EE141

Lecture #14

22

Read Static Noise Margin

 


EECS141

Lecture #14

23

6T-SRAM — Layout

 

这里的PMOS不一定是NMOS的两倍大，
在memory cell的设计中，我们要尽可能
使device小

Compact cell
Bitlines: M2
Wordline: bootstrapped in M3

EECS141



Lecture #14

24

65nm SRAM

□ ST/Philips/Motorola

Access Transistor

  


EECS141

Lecture #14

25

SRAM Column

存在外围电路帮助这个电路进行读取或者写入操作。

 


EECS141

Lecture #14

26

SRAM Array Layout

这种矩阵设计有助于通过共享内存单元的某些元素从而减少节省面积。

 


EECS141

Lecture #14

27

Resistive Pull-Ups

 

Static power dissipation -- Want R_L large
Bit lines precharged to V_{DD} to address t_p problem

EECS141

Lecture #14

28




Memory - DRAM

EECS141

Lecture #14

29

3-Transistor DRAM Cell

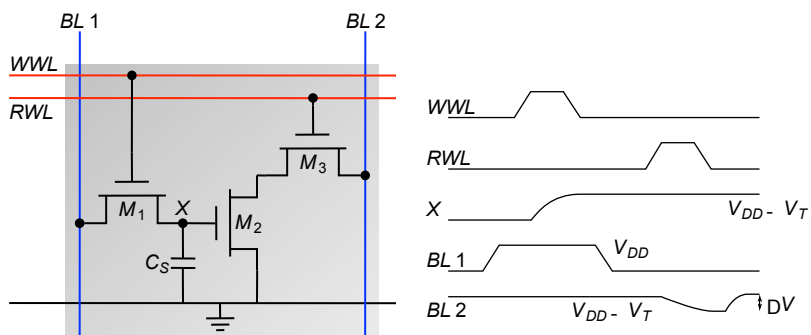

No constraints on device ratios

Reads are non-destructive



Value stored at node X when writing a "1" = $V_{WWL} - V_{Tn}$

EECS141

Lecture #14

30

3T DRAM Layout

 
 


EECS141

Lecture #14

31

1-Transistor DRAM Cell

  

Write: C_s is charged or discharged by asserting WL and BL.
Read: Charge redistribution takes places between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = V_{BIT} - V_{PRE} \frac{C_S}{C_S + C_{BL}}$$


Voltage swing is small; typically around 250 mV.

EECS141

Lecture #14

32

1T1 DRAM Cell

 


Uses Polysilicon-Diffusion Capacitance
Expensive in Area

EECS141

Lecture #14

33

Micrograph of 1T1 DRAM

 


EECS141


Lecture #14

34

Advanced 1T DRAM Cells

 

Trench Cell

 

Stacked-capacitor Cell